

Announcements


- 1) Exam Tuesday Covering
4.3, 4.6, 4.7, 4.10, 5.7,
10.2, 10.5, 10.7
- 2) Practice problems on Canvas
under "Assignments"

RLC Circuits

(Section 5.7)

One resistor, one capacitor,
one inductor

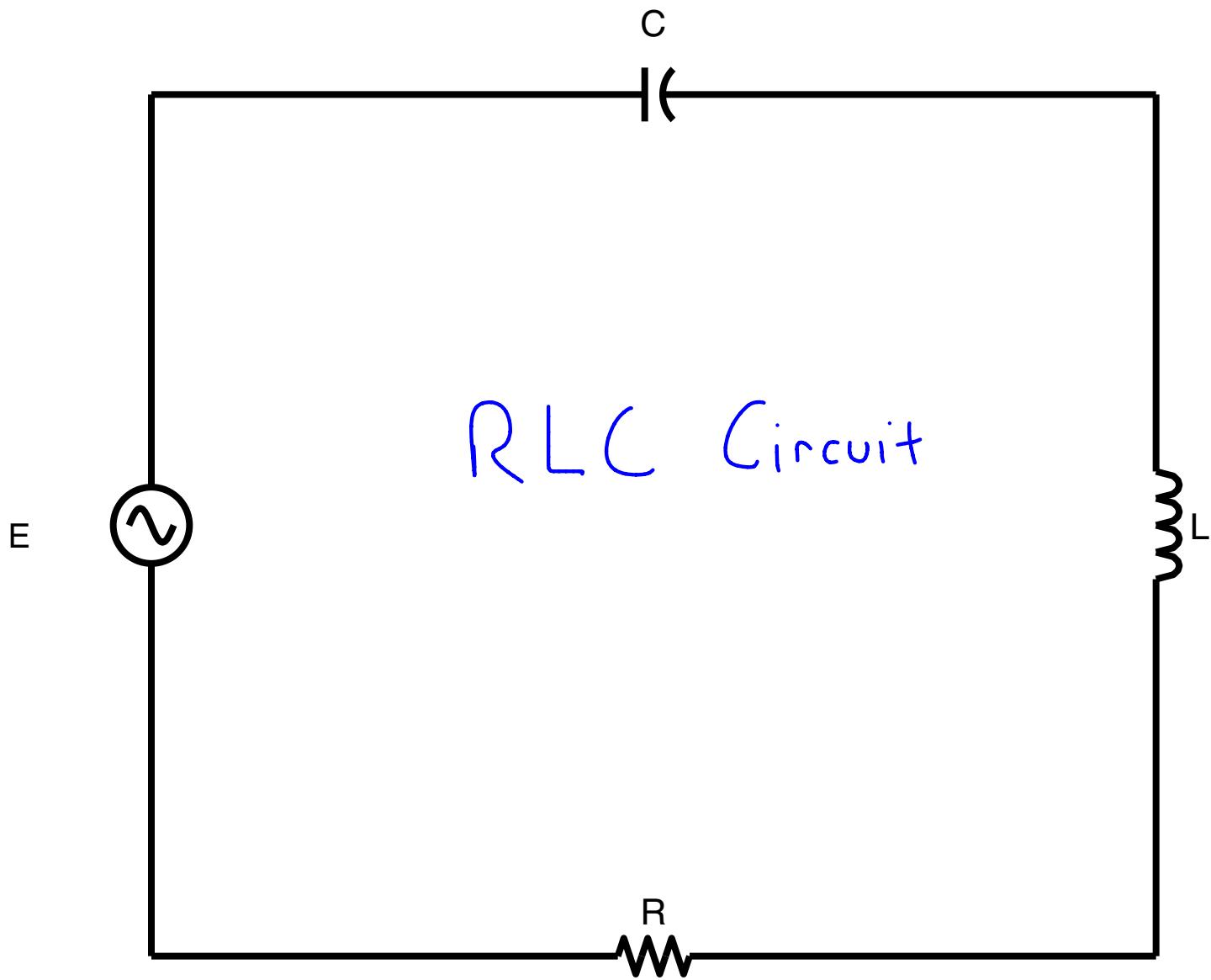No systems of equations,
just one equation!



New Equation

$$E_C + E_R + E_L = E(t)$$

$$E_R = RI$$

$$E_L = L \frac{dI}{dt}$$

$$E_C = \frac{q}{C} \quad \left(\frac{dq}{dt} = I(t) \right)$$

$$L \frac{dI}{dt} + RI + \frac{q}{C} = E(t)$$

Differentiate w.r.t. t

$$L \frac{d^2I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} \frac{dq}{dt} = \frac{dE}{dt}$$

Substitute $\frac{dq}{dt} = I$

$$L \frac{d^2I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = \frac{dE}{dt}$$

Example 3: In a simple RLC

circuit, if $R = 6 \Omega$, $L = 1 H$,

$C = .2 F$, $E(t) = \sin(30t)$,

and the [initial current and

charge on the capacitor are

zero], solve for $I(t)$.

$$\hookrightarrow I(0) = 0, \frac{dI}{dt}(0) = 0$$

Plug into

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = \frac{dE}{dt}$$
$$= 30 \cos(30t)$$

$$\frac{d^2 I}{dt^2} + 6 \frac{dI}{dt} + \frac{1}{0.2} I = 30 \cos(30t)$$

$$\frac{d^2 I}{dt^2} + 6 \frac{dI}{dt} + 5I = 30 \cos(30t)$$

Step 1: Solve homogeneous equation.

Constant coefficients, so

suppose in

$$\frac{d^2I}{dt^2} + 6 \frac{dI}{dt} + 5I = 0,$$

let $I(t) = e^{rt}$. We get

$$e^{rt} (r^2 + 6r + 5) = 0 \text{, so}$$

$$\underbrace{r^2 + 6r + 5}_{} = 0$$

$$(r+5)(r+1)$$

$$r = -1, -5$$

Solutions to homogeneous
equation:

$$y_1(t) = e^{-t}, \quad y_2(t) = e^{-5t}$$

Step 2: Variation of Parameters!

Suppose $y_p(t) = u(t)y_1(t) + v(t)y_2(t)$.

We get

$$u'(t)y_1(t) + v'(t)y_2(t) = 0$$

$$u'(t)y_1'(t) + v'(t)y_2'(t) = 30\cos(30t)$$

$$y_1(t) = e^{-t}, \quad y_1'(t) = -e^{-t}$$

$$y_2(t) = e^{-5t}, \quad y_2'(t) = -5e^{-5t}$$

we get

$$U'(t)e^{-t} + V'(t)e^{-5t} = 0$$

$$-U'(t)e^{-t} - 5V'(t)e^{-5t} = 30\cos(3\pi t)$$

Multiply 1st equation by

$$e^t.$$

$$U'(t) + V'(t)e^{-4t} = 0, \text{ so}$$

$$U'(t) = -V'(t)e^{-4t}$$

Substitute into 2nd equation:

$$v'(t)e^{-5t} - 5v'(t)e^{-5t} = 30\cos(30t),$$

so

$$v'(t) = \frac{30e^{5t}\cos(30t)}{-4}$$

$$\begin{aligned} v'(t) &= -v'(t)e^{-4t} \\ &= \frac{30e^t\cos(30t)}{4} \end{aligned}$$

Using Mathematica, we get

$$v(t) = -\frac{3}{74} e^{5t} (\cos(30t) + 6 \sin(30t))$$

$$u(t) = \frac{15}{1802} e^t (\cos(30t) + 30 \sin(30t))$$

and

$$y_p(t) = y_1(t)u(t) + y_2(t)v(t)$$

$$= \boxed{\frac{-6(179 \cos(30t) - 36 \sin(30t))}{33,337}}$$

So

$$I(t) = y_p(t) + C_1 y_1(t) + C_2 y_2(t)$$

$$= \frac{-6(179\cos(30t) - 36\sin(30t))}{33,337}$$

$$+ C_1 e^{-t} + C_2 e^{-5t}$$

Now use initial conditions.

$$I(0) = 0, I'(0) = 0$$

$$\underline{I(0)=0}$$

$$0 = -\frac{6(17^9)}{33,337} + C_1 + C_2$$

$$C_2 = -C_1 + \frac{1074}{33,337}$$

$$\underline{I'(0)=0}$$

$$I'(t) = -C_1 e^{-t} - 5C_2 e^{-5t} + 6 \left(\frac{5370 \sin(3\omega t) + 1080 \cos(3\omega t)}{33337} \right)$$

$$I'(0) = -C_1 - 5C_2 + \frac{6(1080)}{33337}$$

$$= 0$$

$$0 = -C_1 - 5 \left(\frac{1074}{33337} - C_1 \right) + \frac{6480}{33337}$$

$$= 4C_1 + \frac{1110}{3337}$$

$$C_1 = \frac{-555}{2(3337)}$$

$$C_2 = -C_1 + \frac{1074}{3337}$$

$$= \frac{2703}{2(3337)}$$

$$I(t) = \frac{-555}{2(3337)} e^{-t} + \frac{2703}{2(3337)} e^{-5t}$$

$$-6 \left(\frac{179 \cos(30t) - 36 \sin(30t)}{3337} \right)$$