

Announcements :

1) HW #2 Supplement due
tomorrow

2) Quiz Thursday over
today's material.


Circuit Problems


(section 3.5)

We will only consider simple circuits with a voltage source (battery or generator), a resistor, and either an inductor or capacitor (but not both!)

One inductor = RL Circuit

One Capacitor = RC Circuit

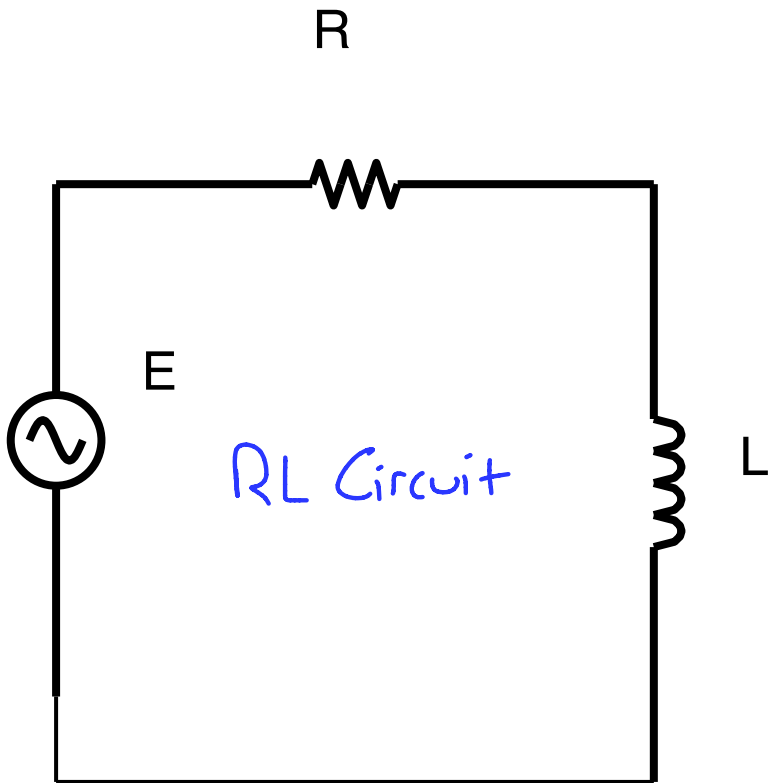

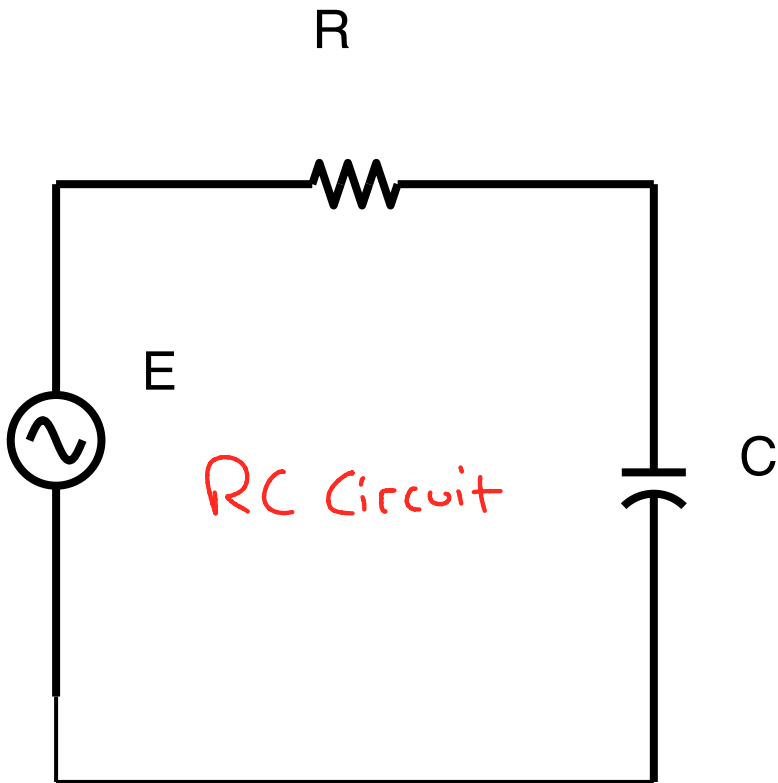

Here are a bunch of laws

1) Kirchoff's Current: the sum of all currents flowing into any junction point is zero

2) Kirchoff's Voltage: the sum of the instantaneous changes in potential (voltage drops) around any closed loop is zero

3) Ohm's Law : if E_R is the voltage drop through a resistor and I is the current,

$$E_R = RI$$

4) Faraday's / Lenz's Law :

$$\mathcal{E} = - \frac{d\Phi_B}{dt}$$

where \mathcal{E} = electromotive force,

Φ_B = magnetic flux

Using this, we can show

$$E_L = L \frac{dI}{dt}$$

where E_L is the voltage drop across an inductor

5) If q is the electrical charge on a capacitor,

$$E_C = \frac{1}{C} q$$

where E_C is the voltage drop across a capacitor

In an RL Circuit

Kirchoff's Voltage Law implies

$$E(t) = E_L + E_R$$

where $E(t)$ is the voltage in the circuit at time t

from Faraday's Law,

$$E_L = L \frac{dI}{dt}, \text{ substitute.}$$

We get

$$E(t) = L \frac{dI}{dt} + E_R.$$

Using Ohm's Law,

$$E(t) = L \frac{dI}{dt} + R I(t)$$

Can solve using integrating factors.

Example 1 : If $R = 1\Omega$,

$L = 0.01$ H (Henry) and

$E(t) = \sin(100t)$, solve

for I in our equation

$$E(t) = L \frac{dI}{dt} + RI(t).$$

We have

$$\sin(100t) = .01 \frac{dI}{dt} + I(t).$$

Rewrite in standard form:

$$100 \sin(100t) = \frac{dI}{dt} + 100I(t).$$

Multiply both sides by the

integrating factor $\mu(t)$ where

$$\frac{d}{dt} (\mu(t) I(t))$$

$$= \mu(t) \frac{dI}{dt} + 100\mu(t) I(t)$$

Solve for $\mu(t)$: By the product rule,

$$\mu'(t) = 100\mu(t),$$

So $\mu(t) = e^{100t}$.

multiplying by $e^{100t} = u(t)$,

$$100 e^{100t} \sin(100t)$$

$$= e^{100t} \frac{dI}{dt} + 100 e^{100t} I(t)$$

$$= \frac{d}{dt} (e^{100t} I(t)).$$

Integrate both sides with respect to t .

Integrating, we get

$$\int 100e^{100t} \sin(100t) dt$$

$$= \int \frac{d}{dt} (e^{100t} I(t)) dt$$

$$= e^{100t} I(t) + C.$$

How to solve

$$\int 100e^{100t} \sin(100t) dt ?$$

$$\int 100 e^{100t} \sin(100t) dt$$

$$u = 100t$$

$$du = 100 dt \quad \text{gives}$$

$$\int e^u \sin(u) du.$$

Integrate by parts:

$$w = \sin(u) \quad v = e^u$$

$$dw = \cos(u) du \quad dv = e^u du$$

We get

$$\int e^u \sin(u) du$$

$$= e^u \sin(u) - \int e^u \cos(u) du$$

Persevere! Stick to your choices
of w, v .

$$w = \cos(u)$$

$$v = e^u$$

$$dw = -\sin(u) du$$

$$dv = e^u du$$

Don't choose $w = e^u$!

$$\int e^u \sin(u) du$$

$$= e^u \sin(u)$$

$$- (e^u \cos(u) + \int e^u \sin(u) du)$$

$$= e^u (\sin(u) - \cos(u)) - \int e^u \sin(u) du$$

Add $\int e^u \sin(u) du$ to both sides!

We get

$$2 \int e^u \sin(u) du$$

$$= e^u (\sin(u) - \cos(u)),$$

So $\int e^u \sin(u) du$

$$= \frac{e^u (\sin(u) - \cos(u))}{2}$$

Substituting $u = 100t$,

$$\frac{e^{100t} (\sin(100t) - \cos(100t))}{2}$$

$$= \int 100 e^{100t} \sin(100t) dt$$

$$= e^{100t} I(t) + C \quad \begin{array}{l} \text{from} \\ \text{before} \end{array}$$

Using initial condition $I(u) = 0$

Using initial condition $I(0)=0$,

$$-\frac{1}{2} = C, \text{ and so}$$

$$I(t) = \frac{\sin(100t) - \cos(100t)}{2} + \frac{1}{2}e^{100t}$$

Capacitors are Easier!

The our equation

$$E(t) = E_R + E_C$$

$$= RI(t) + E_C$$

and substituting

$$E_C = \frac{q}{C} ,$$

$$E(t) = RI(t) + \frac{q}{C}$$

There are no derivatives,
so this is not a calculus
problem!