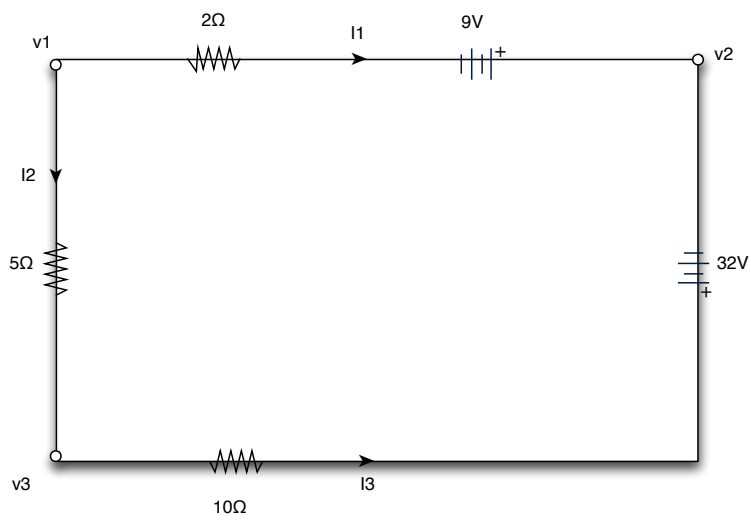


## Math 227 Assignment 3 Supplement

Due Friday, February 1

1) (5 points each) Calculate the values of the indicated currents in the diagrams below.

a)



b)

