

Announcements

1) Webwork #2, 4


"perpendicular" = "orthogonal"

2) Math Colloquium today

3-4 in CB 2064

"p-adic numbers"

Recall Example 4 from
last class

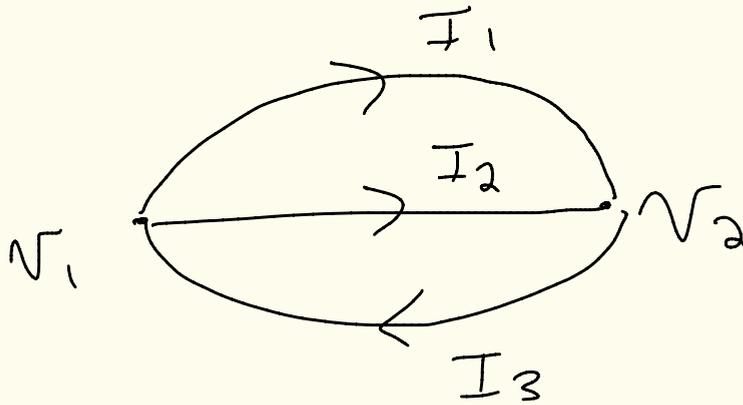

Edge-Node Incidence Matrix

$$A = \begin{bmatrix} -1 & 1 \\ -1 & 1 \\ 1 & -1 \end{bmatrix}$$

Kirchhoff's Current Law

- I_1, I_2, \dots, I_m the currents along each edge (in amperes).
- f_1, f_2, \dots, f_n external current sources associated to each node
- $A =$ edge-node incidence matrix

$$A^t \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_m \end{bmatrix} = \begin{bmatrix} f_1 \\ f_2 \\ \vdots \\ f_n \end{bmatrix}$$

Current Law

What it says:

" The current flowing into any node is equal to the current flowing out of the node. "

Note: no external
current sources

$$f_1 = f_2 = \dots = f_n = 0$$

for every node.

In that case, Kirchoff's
Current Law becomes

$$A^t \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_m \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

Example 4 Again

$$A = \begin{bmatrix} -1 & 1 \\ -1 & 1 \\ 1 & -1 \end{bmatrix} \quad (3 \times 2)$$

$$A^t = \begin{bmatrix} -1 & -1 & 1 \\ 1 & 1 & -1 \end{bmatrix} \quad (2 \times 3)$$

We assume no external current sources, so we get

$$\overbrace{\begin{bmatrix} -1 & -1 & 1 \\ 1 & 1 & -1 \end{bmatrix}}^{A^t} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

To solve, put the following matrix:

$$\begin{bmatrix} -1 & -1 & 1 & 0 \\ 1 & 1 & -1 & 0 \end{bmatrix}$$

in rref.

We'd get

$$\begin{bmatrix} 1 & 1 & -1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

This says

$$I_1 + I_2 - I_3 = 0,$$

$$\text{So } I_3 = I_1 + I_2,$$

but we have infinitely many solutions depending on our choices for I_1, I_2 .

Ohm's Law

R_1, R_2, \dots, R_m resistance
along each edge (in Ohms).

b_1, b_2, \dots, b_m battery strength
along each edge (in volts)

Let R be the $m \times m$

diagonal matrix

$$\begin{bmatrix} R_1 & 0 & \dots & 0 \\ 0 & R_2 & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & \dots & 0 & R_m \end{bmatrix} = R$$

Then

$$R \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_m \end{bmatrix} + A \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_m \end{bmatrix}$$

Ohm's Law

Note: V_1, V_2, \dots, V_n are now the electric potentials (voltage) at each node. We are assuming current flows from positive to negative.

If we write

$$\mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_m \end{bmatrix} \quad \text{and}$$

$$\mathbf{V} = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_m \end{bmatrix} - A \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_n \end{bmatrix},$$

then subtracting $A \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_n \end{bmatrix}$

from both sides of Ohm's Law

gives $\mathbf{R} \mathbf{I} = \mathbf{V}$

In words,


"Current times resistance
is equal to the
voltage".

Final Look at Example 4

Battery: 

small line is the positive end

Resistor: 

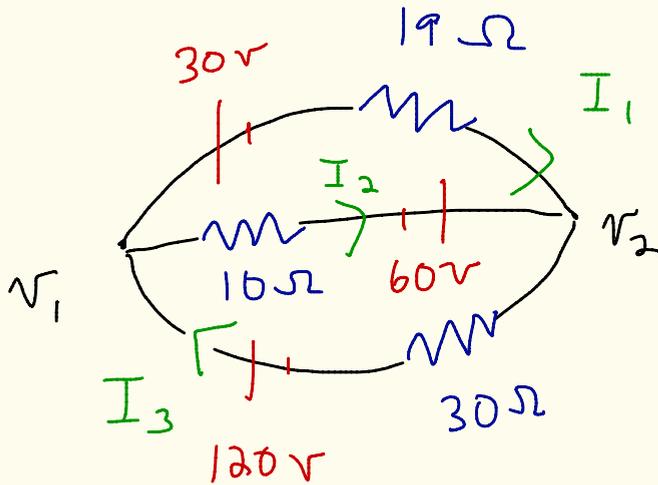

" Ω " = Ohms, " V " = volts

Ohm's Law

$$R \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} + A \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix}$$

I_1, I_2, I_3, V_1, V_2 are the

Unknowns.

$$R = \begin{bmatrix} 19 & 0 & 0 \\ 0 & 10 & 0 \\ 0 & 0 & 30 \end{bmatrix}$$

$$A = \begin{bmatrix} -1 & 1 \\ -1 & 1 \\ 1 & -1 \end{bmatrix}$$

$$b_1 = -30 \text{ (since current flows the wrong way)}$$

$$b_2 = 60$$

$$b_3 = 120$$

We then have

$$\begin{bmatrix} 19 & 0 & 0 \\ 0 & 10 & 0 \\ 0 & 0 & 30 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} + \begin{bmatrix} -1 & 1 \\ -1 & 1 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$= \begin{bmatrix} -30 \\ 60 \\ 120 \end{bmatrix}$$

How to use a single matrix to solve this problem?

We make a huge matrix that incorporates both laws:

$$\begin{bmatrix}
 \overset{m \times m}{\underbrace{R}} & \overset{m \times n}{\underbrace{A}} \\
 \underbrace{A^t}_{n \times m} & \text{(block of zeros)}
 \end{bmatrix}
 \begin{bmatrix}
 I_1 \\
 I_2 \\
 \vdots \\
 I_m
 \end{bmatrix}$$

$$\parallel
 \begin{bmatrix}
 b_1 \\
 b_2 \\
 \vdots \\
 b_m
 \end{bmatrix}$$

We use this to finish

example

U

$$\left[\begin{array}{ccc|cc} \hline 19 & 6 & 0 & -1 & 1 \\ 0 & 10 & 0 & -1 & 1 \\ 6 & 0 & 30 & 1 & -1 \\ \hline -1 & -1 & 1 & 0 & 0 \\ 1 & 1 & -1 & 0 & 0 \\ \hline \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ v_1 \\ v_2 \end{bmatrix}$$

A^t

$$= \begin{bmatrix} -30 \\ 60 \\ 120 \\ 6 \\ 0 \end{bmatrix}$$

The solution comes
from row-reducing

$$\left[\begin{array}{cccccc} 19 & 0 & 0 & -1 & 1 & -30 \\ 0 & 10 & 0 & -1 & 1 & 60 \\ 0 & 0 & 30 & 1 & -1 & 120 \\ -1 & -1 & 1 & 0 & 0 & 0 \\ 1 & 1 & -1 & 0 & 0 & 0 \end{array} \right]$$

rref is

$$\left[\begin{array}{cccccc} 1 & 0 & 0 & 0 & 0 & -90/53 \\ 0 & 1 & 0 & 0 & 0 & 306/53 \\ 0 & 0 & 1 & 0 & 0 & 216/53 \\ 0 & 0 & 0 & 1 & -1 & -120/53 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{array} \right]$$

We get

$$I_1 = -90/53$$


$$I_2 = 306/53$$

$$I_3 = 216/53$$

$$v_1 - v_2 = -120/53$$

We can only solve for v_1 in terms of v_2 , but this makes sense.

Another Example

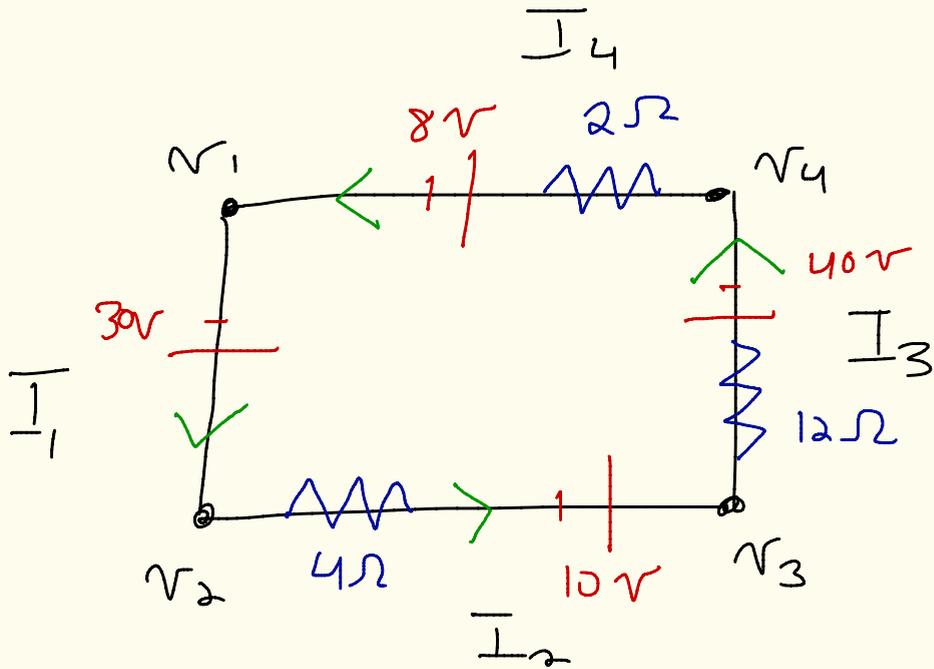

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 1 \\ 1 & 0 & 0 & -1 \end{bmatrix}$$

$$A^t = \begin{bmatrix} -1 & 0 & 0 & 1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix}$$

$$R = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 4 & 0 & 0 \\ 0 & 0 & 12 & 0 \\ 0 & 0 & 0 & 2 \end{bmatrix}$$

$$b_1 = 30, b_2 = 10, b_3 = -40, b_4 = -8$$

Row reduce

$$\left[\begin{array}{cc|c} R & A & b_1 \\ & & b_2 \\ & & b_3 \\ & & b_4 \\ A^t & (\text{zeros}) & 0 \\ & & 0 \\ & & 0 \end{array} \right]$$

$$= \left[\begin{array}{cccc|cccc|c} 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 & 30 \\ 0 & 4 & 0 & 0 & 0 & -1 & 1 & 0 & 10 \\ 0 & 0 & 12 & 0 & 0 & 0 & -1 & 1 & -40 \\ 0 & 0 & 0 & 2 & 1 & 0 & 0 & -1 & -8 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 \end{array} \right]$$

ref is

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -4/9 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & -4/9 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & -4/9 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & -4/9 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -1 & -64/9 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & -1 & 206/9 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & -1 & 104/3 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\text{So } I_1 = I_2 = I_3 = I_4 = -4/9$$

$$r_1 = -64/9 + r_4$$

$$r_2 = 206/9 + r_4$$

$$r_3 = 104/3 + r_4$$