

ECE 512 Computer Assignment #1

Objective:

The objective of this assignment is to design and simulate simple passive first order and second order filters.

- 1) Design a first order lowpass filter with a cutoff frequency of 10 kHz. The available capacitor value is 10 nF.
 - a) Verify your design using Pspice by plotting the magnitude (in dB) and phase responses.
 - b) What is the frequency where the magnitude response is -12 db?
 - c) Find the frequency where the phase response is -45° .

- 2) It is required to design a second order highpass filter to filter out the signal $x_1(t)$ and pass the signals $x_2(t)$ and $x_3(t)$ from the composite signal $x(t) = x_1(t) + x_2(t) + x_3(t)$,

where

$$x_1(t) = \cos(2000\pi t + \pi/3), \quad x_2(t) = 10 \cos(10,000\pi t) \text{ and } x_3(t) = 11 \cos(20,000\pi t + \pi/4).$$

- a) What values of cutoff frequency and Q values do you choose? Give reasons. From part a), calculate the values of the circuit elements needed, assuming the capacitor value available is in the nano Farad range.
- b) Give an expression of the output of the filter at steady state ($y_{ss}(t)$).

- 3) It is required to design a filter to pass the frequency band described by $95 \text{ kHz} \leq f \leq 105 \text{ kHz}$ and filter out the rest bands. Assume that the capacitor used is 100 pF.

- a) Calculate an appropriate center frequency and quality factor.
- b) Give the complete design of the filter. Hence, verify the frequency response through simulation.
- c) If the value of the capacitor c is changed by $\pm 5\%$, $\pm 10\%$ and $\pm 20\%$ of its nominal value, find the corresponding percentage change in the center frequency (f_o) and quality factor (Q). Hence, plot the percentage change in f_o and Q versus percentage change in the value of c .

Verify your results through simulations.